

Figure 1: THD of input line current

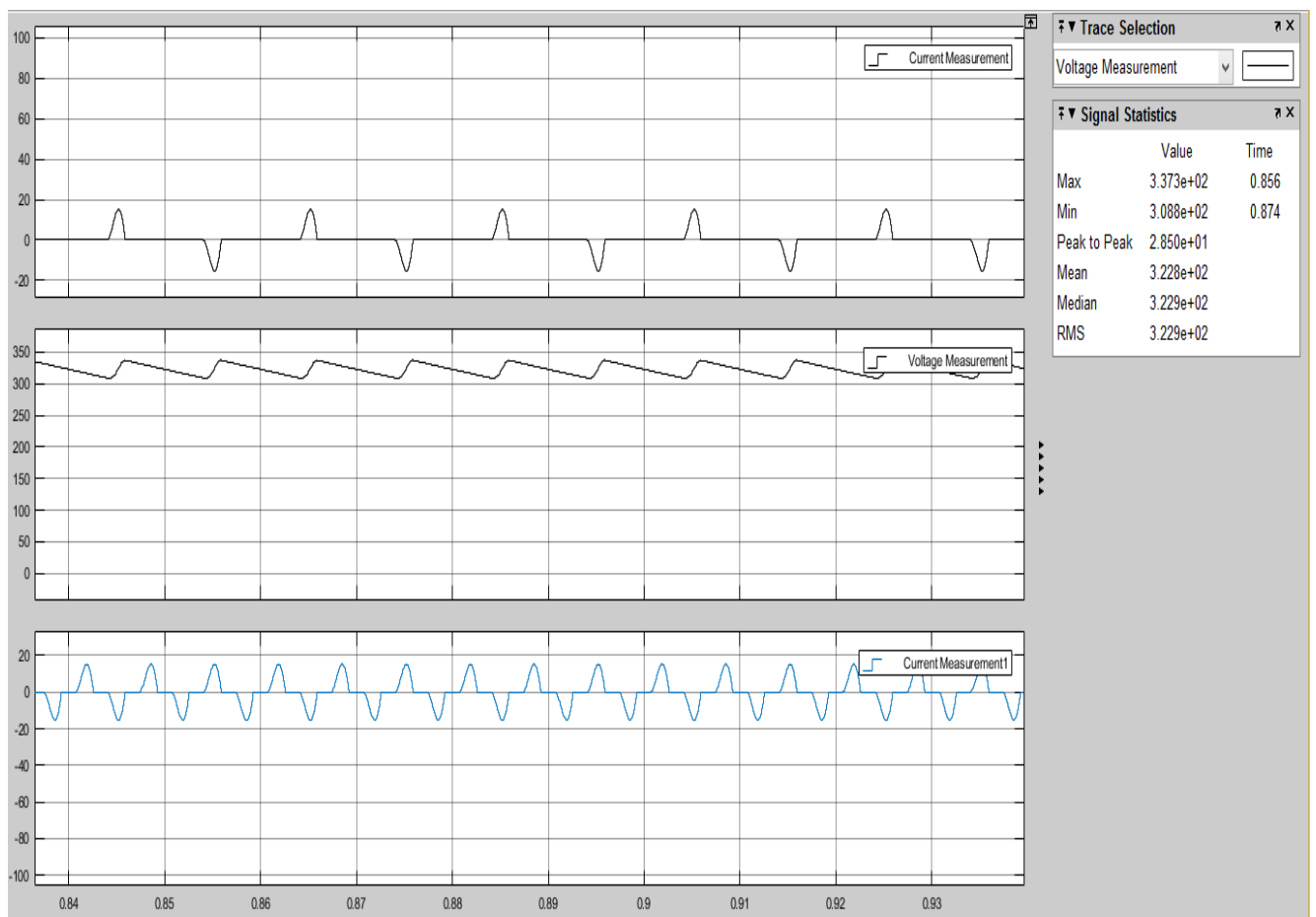


Figure 2: Waveforms of input line current, neutral line current and output voltage with L_s

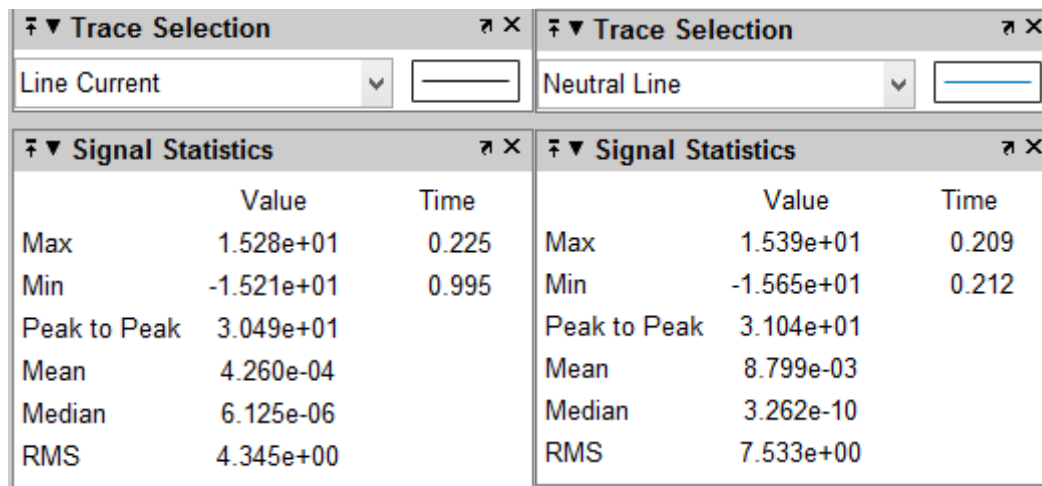


Figure 3: RMS values of input line current and neutral line

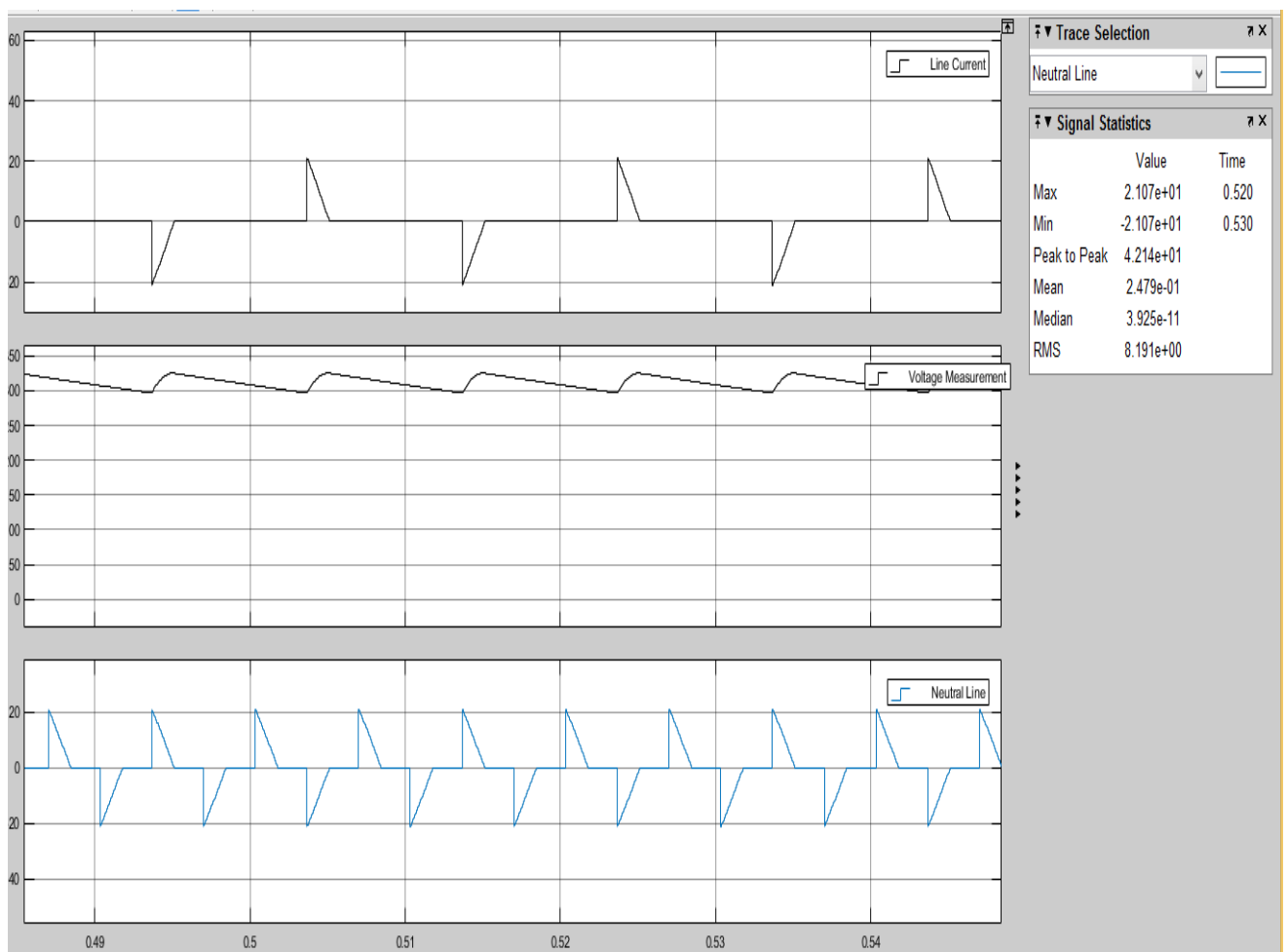


Figure 4: Waveforms of input line current, neutral line current and output voltage without L_s